ELCT 222

Signals and Systems Computer Assignment 3

Important:

- This assignment must be typed (e.g., a Word document) no handwritten work accepted.
- Providing only MATLAB code or only MATLAB output without any discussion will receive 0 points.
- Unclear or illegible work will not receive full credit.
- For answers, provide your discussions or your approach to solving the problems and describe in clear English how your routine works in a few sentences.
- Include MATLAB code at the END of the assignment as an appendix.
- Label all axes in MATLAB.
- 1. For two cases (i) RC = 0.1 and (ii) RC = 1:
 - a. (20 pts) Calculate the frequency response analytically
 - b. (20 pts) (20 pts) Plot the frequency response (magnitude and phase on different plots) as a function of f in Hertz between 0 to 10 Hertz. Which one does suppress the higher frequency tones better?
 - c. (20 pts) Compute the output y(t) if the input to the system is given by

$$x(t) = 1 + \cos(5t) + \cos(10t) + \cos(15t)$$

- d. (20 pts) Plot both absolute value of the input and output signals
- e. (20 pts) Discuss the behavior of the circuit to different tones based on the plots above.

